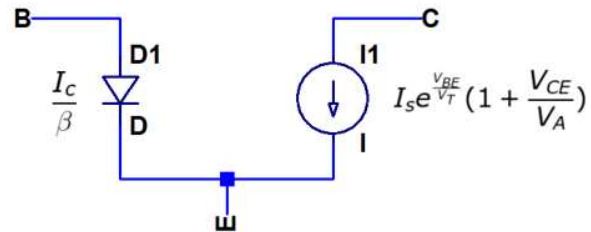


BJT


$$I_S = \frac{A_E q D_n n_i^2}{N_B W_B}$$

Ae=area, q=charge, D_n =diffusion constant, n_i =electron density
 N_b =base acceptors, W_b =base width


Large Signal



Small Signal

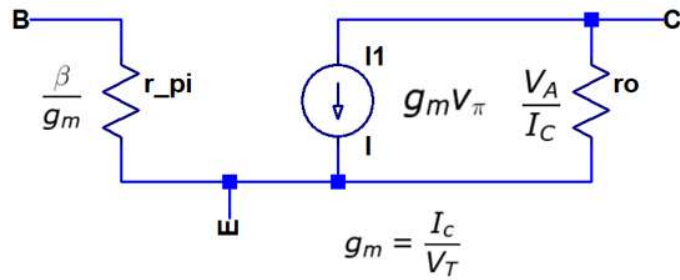


Diode-Connected

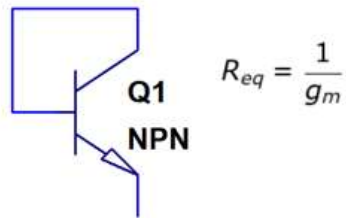

$$R_{eq} = \frac{1}{g_m}$$

Common-Emitter

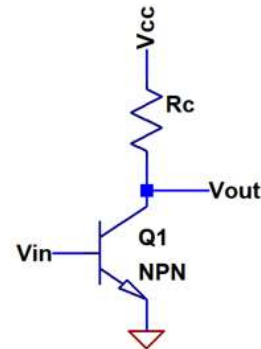


$$A_v = -g_m(R_c \parallel r_o)$$

$$R_{in} = r_\pi$$

$$R_{out} = R_c \parallel r_o$$

Common-Emitter with Degeneration

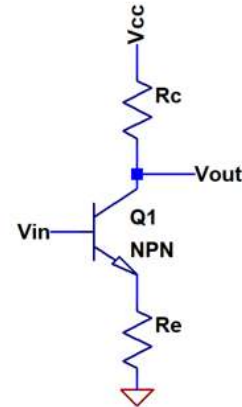


$$A_v = \frac{-(R_c \parallel r_o)}{\frac{1}{g_m} + R_e}$$

$$R_{in} = r_\pi + (\beta + 1)R_e$$

$$R_{out} = R_c \parallel r_o$$

BJT Cascode

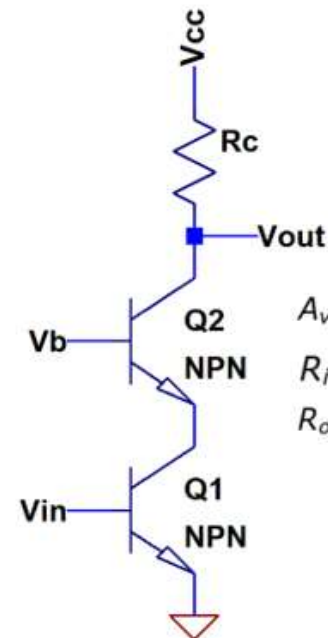


$$A_v = -g_{m1}(R_c \parallel [g_{m2}r_{o2}(r_{o1} \parallel r_{\pi 2}) + r_{o1} \parallel r_{\pi 2}])$$

$$R_{in} = r_\pi$$

$$R_{out} = R_c \parallel [g_{m2}r_{o2}(r_{o1} \parallel r_{\pi 2}) + r_{o1} \parallel r_{\pi 2}]$$

Common-Base

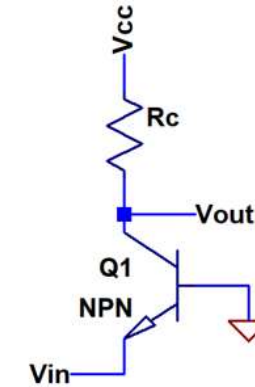


$$A_v = g_m(R_c \parallel r_o)$$

$$R_{in} = \frac{1}{g_m}$$

$$R_{out} = (R_c \parallel r_o)$$

Common-Collector (Emitter Follower)

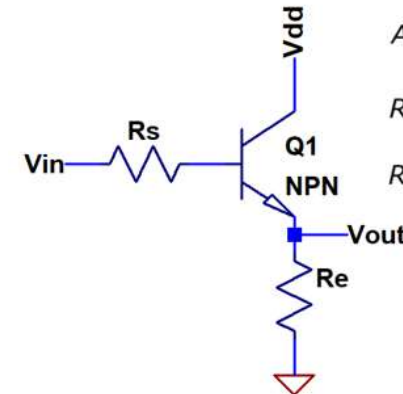

$$A_v = \frac{R_e}{\frac{1}{g_m} + R_e}$$

$$R_{in} = r_\pi + (\beta + 1)R_e$$


$$R_{out} = R_e \parallel (\frac{R_s}{\beta + 1} + \frac{1}{g_m})$$

MOSFET


$$K = \frac{1}{2} \mu_n C_{ox} \frac{W}{L}$$

μ_n =carrier mobility, C_{ox} =capacitance per area, W =width, L =length


Large Signal

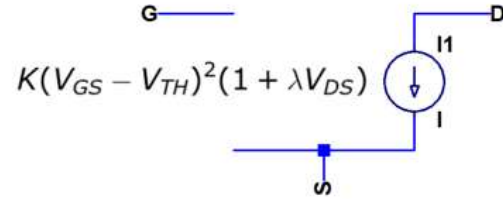


Small Signal

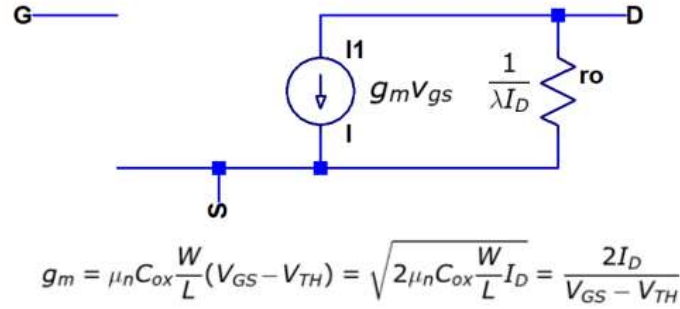

Diode-Connected

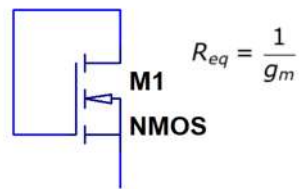

Common-Source

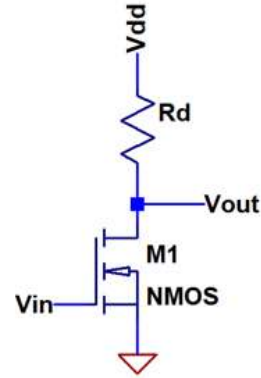


$$A_v = -g_m(R_d || r_o)$$

$$R_{in} = \infty$$

$$R_{out} = R_d || r_o$$

Common-Source with Degeneration

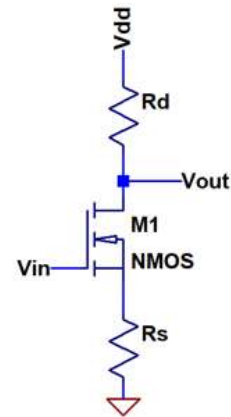


$$A_v = \frac{-(R_d || r_o)}{\frac{1}{g_m} + R_s}$$

$$R_{in} = \infty$$

$$R_{out} = (g_m R_s + 1) r_o$$

Common-Gate

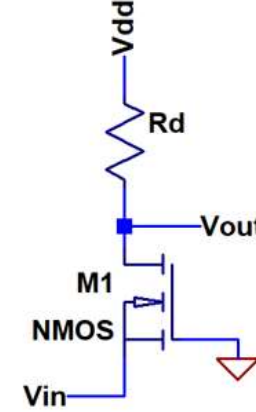


$$A_v = g_m(R_d || r_o)$$

$$R_{in} = \frac{1}{g_m}$$

$$R_{out} = R_d || r_o$$

Common-Drain (Source Follower)

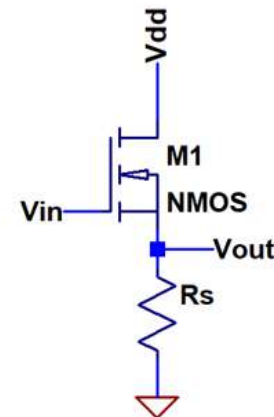


$$A_v = \frac{r_o || R_s}{\frac{1}{g_m} + r_o || R_s}$$

$$R_{in} = \infty$$

$$R_{out} = \frac{1}{g_m} || r_o || R_s$$

MOSFET Cascode

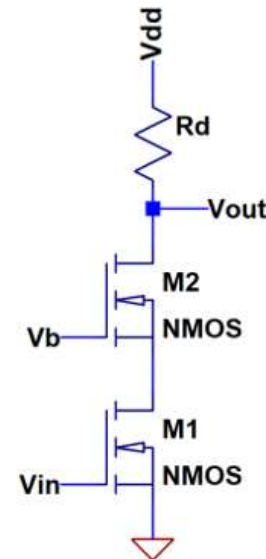

$$A_v = -g_{m2}(R_d || [(1 + g_{m1}r_{o1})r_{o2} + r_{o1}])$$

$$R_{in} = \infty$$

$$R_{out} = R_d || [(1 + g_{m1}r_{o1})r_{o2} + r_{o1}]$$